

Τρανζίστορ N-MOS	Διπολικό τρανζίστορ (BJT) ($r_x \equiv r_{bb'}$, $r_\pi \equiv r_{b'e}$, $r_e \equiv r_d$)
$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2 \left(1 + \frac{v_{DS}}{V_A}\right)$ $= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} v_{OV}^2 \left(1 + \frac{v_{DS}}{V_A}\right)$ $k'_n = \mu_n C_{ox}$ $g_m = (\mu_n C_{ox}) \left(\frac{W}{L}\right) V_{OV} \quad g_m = 2I_D / V_{OV} $ $r_o = V_A / I_D = V_A' L / I_D$ $r_{in} = \infty \quad (\text{στο σινεχές})$ $\omega_T = g_m / (C_{gs} + C_{gd})$ $C_{ov} = W L_{ov} C_{ox}$ $C_{sb} = \frac{C_{sb0}}{\sqrt{1 + \frac{V_{SB}}{V_0}}} \quad C_{db} = \frac{C_{db0}}{\sqrt{1 + \frac{V_{DB}}{V_0}}}$ <p>Τριοδική (ωμική):</p> $C_{gs} = C_{gd} = \frac{1}{2} W L C_{ox}$ <p>Κορεσμού:</p> $\left. \begin{aligned} C_{gs} &= \frac{2}{3} W L C_{ox} \\ C_{gd} &= 0 \end{aligned} \right\}$ <p>Αποκοπής:</p> $\left. \begin{aligned} C_{gs} &= C_{gd} = 0 \\ C_{gb} &= W L C_{ox} \end{aligned} \right\}$	$i_C = I_S e^{v_{BE}/V_T} \left(1 + \frac{v_{CE}}{V_A}\right) \quad r_e = \frac{\alpha}{g_m} \quad r_\pi = \frac{\beta}{g_m}$ $g_m = \frac{I_C}{V_T} \quad r_e = \frac{V_T}{I_E} = \alpha \left(\frac{V_T}{I_C}\right) \quad r_\pi = \frac{V_T}{I_B} = \beta \left(\frac{V_T}{I_C}\right) \quad r_o = \frac{ V_A }{I_C}$ $g_m = \frac{\alpha}{r_e} \quad r_\pi = (\beta + 1) r_e \quad g_m + \frac{1}{r_\pi} = \frac{1}{r_e}$ $\beta = \frac{\alpha}{1 - \alpha} \quad \alpha = \frac{\beta}{\beta + 1} \quad \beta + 1 = \frac{1}{1 - \alpha}$ $C_\pi + C_\mu = \frac{g_m}{2\pi f_T} \quad C_\pi = C_{de} + C_{je} \quad C_{de} = \tau_F g_m \quad C_{je} \approx 2C_{je0}$ $C_\mu = C_{jc0} / \left(1 + \frac{V_{CB}}{V_{0c}}\right)^m, \quad m \approx 0.3 - 0.5$ $\omega_\beta = \frac{1}{(C_\pi + C_\mu) r_\pi}$ $\omega_T = \beta_0 \omega_\beta$

Διαφορικός ενισχυτής με MOS	Διαφορικός ενισχυτής με BJT
$v_{CMmax} = V_t + V_{DD} - \frac{I}{2} R_D$ $v_{CMmin} = -V_{SS} + V_{CS} + V_t + V_{OV}$ $i_{D1} = \frac{I}{2} + \left(\frac{I}{V_{OV}}\right) \left(\frac{v_{id}}{2}\right) \sqrt{1 - \left(\frac{v_{id}/2}{V_{OV}}\right)^2}$ $i_{D2} = \frac{I}{2} - \left(\frac{I}{V_{OV}}\right) \left(\frac{v_{id}}{2}\right) \sqrt{1 - \left(\frac{v_{id}/2}{V_{OV}}\right)^2}$ $i_d = \left(\frac{I}{V_{OV}}\right) \left(\frac{v_{id}}{2}\right) \quad -\sqrt{2} V_{OV} \leq v_{id} \leq \sqrt{2} V_{OV}$ <p>Διαφορική έξοδος:</p> $A_d \equiv \frac{v_{o2} - v_{o1}}{v_{id}} = g_m R_D \quad CMRR = \infty$ $v_o = v_{o2} - v_{o1} = g_m (R_D \parallel r_o) v_{id}$	$i_{E1} = \frac{I}{1 + e^{-v_{id}/V_T}}$ $i_{E2} = \frac{I}{1 + e^{v_{id}/V_T}}$ <p>Διαφορική έξοδος:</p> $A_d = \frac{v_{c1} - v_{c2}}{v_d} = -g_m R_C \quad A_d = -g_m (R_C \parallel r_o)$ $A_d = -\frac{\alpha(2R_C)}{2r_e + 2R_e} \approx -\frac{R_C}{r_e + R_e}$ $R_{id} = (\beta + 1)(2r_e + 2R_e) \quad CMRR = \infty$ $R_{icm} \approx (\beta + 1) \left(R_{EE} \parallel \frac{r_o}{2}\right)$ $CMRR = \left \frac{A_d}{A_{cm}}\right = (2g_m R_{EE}) / \left(\frac{\Delta R_C}{R_C}\right)$

$CMRR = \left \frac{A_d}{A_{cm}} \right = (2g_m R_{SS}) / \left(\frac{\Delta R_D}{R_D} \right)$ $CMRR = \left \frac{A_d}{A_{cm}} \right = (2g_m R_{SS}) / \left(\frac{\Delta g_m}{g_m} \right)$ <p>Απλή έξοδος:</p> $ A_d = \frac{1}{2} g_m R_D \quad A_{cm} = \frac{R_D}{2R_{SS}}$ $CMRR = \left \frac{A_d}{A_{cm}} \right = g_m R_{SS}$ <p>Τάση εκτροπής εισόδου:</p> $V_{OS} = \sqrt{\left(\frac{V_{OV}}{2} \frac{\Delta R_D}{R_D} \right)^2 + \left(\frac{V_{OV}}{2} \frac{\Delta(W/L)}{W/L} \right)^2 + (\Delta V_t)^2}$ <p>Με ενεργό φορτίο:</p> $R_o \equiv \frac{v_x}{i_x} = r_{o2} \parallel r_{o4}$ $A_d \equiv \frac{v_o}{v_{id}} = G_m R_o = g_m (r_{o2} \parallel r_{o4})$ $A_{cm} \equiv \frac{v_o}{v_{icm}} = -\frac{1}{2R_{SS}} \frac{r_{o4}}{1 + g_{m3} r_{o3}}$ $CMRR = (g_m r_o)(g_m R_{SS})$	<p>Απλή έξοδος:</p> $A_d = \frac{v_{c1}}{v_d} = -\frac{1}{2} g_m R_C \quad A_{cm} = -\frac{\alpha R_C}{2R_{EE}}$ $CMRR = \left \frac{A_d}{A_{cm}} \right \approx g_m R_{EE}$ <p>Τάση εκτροπής εισόδου:</p> $V_{OS} = V_T \sqrt{\left(\frac{\Delta R_C}{R_C} \right)^2 + \left(\frac{\Delta I_S}{I_S} \right)^2}$ <p>Ρεύμα εκτροπής εισόδου:</p> $I_{OS} = I_B \left(\frac{\Delta \beta}{\beta} \right), \text{ όπου: } I_B \equiv \frac{I_{B1} + I_{B2}}{2} = \frac{I}{2(\beta + 1)}$ <p>Με ενεργό φορτίο:</p> $R_o \equiv \frac{v_x}{i_x} = r_{o2} \parallel r_{o4}$ $A_d \equiv \frac{v_o}{v_{id}} = G_m R_o = g_m (r_{o2} \parallel r_{o4})$ $A_{cm} \equiv -\frac{r_{o4}}{\beta_3 R_{EE}} \quad CMRR = \frac{1}{2} \beta_3 g_m R_{EE}$ $V_{OS} = -\frac{\alpha I / \beta_P}{\alpha I / 2V_T} = -\frac{2V_T}{\beta_P}$
--	--

Απόκριση στις χαμηλές συχνότητες

<p>Κοινής πηγής:</p> $A_M \equiv \frac{V_o}{V_{sig}} = -\frac{R_G}{R_G + R_{sig}} g_m (r_o \parallel R_D \parallel R_L)$ $\omega_{P1} = \omega_0 = \frac{1}{C_{C1}(R_G + R_{sig})}$ $\omega_{P2} = \frac{g_m}{C_S}$ $\omega_{P3} = \frac{1}{C_{C2}(R_D + R_L)}$	<p>Κοινού εκπομπού:</p> $A_M = \frac{V_o}{V_{sig}} = -\frac{(R_B \parallel r_\pi)}{(R_B \parallel r_\pi) + R_{sig}} g_m (r_o \parallel R_C \parallel R_L)$ $\omega_{P1} = \frac{1}{C_{C1}[(R_B \parallel r_\pi) + R_{sig}]}$ $\omega_{P2} = \frac{1}{C_E \left[r_e + \frac{R_B \parallel R_{sig}}{\beta + 1} \right]}$ $\omega_{P3} = \frac{1}{C_{C2}(R_C + R_L)}$
--	--

Απόκριση στις υψηλές συχνότητες

<p>Κοινής πηγής:</p> $f_H = \frac{\omega_H}{2\pi} = \frac{1}{2\pi C_{in} R'_{sig}} \quad R'_L = r_o \parallel R_D \parallel R_L$ $C_{in} = C_{gs} + C_{eq} = C_{gs} + C_{gd}(1 + g_m R'_L)$ <p>Κοινής πηγής με ενεργό φορτίο:</p> $A_M = -g_m R'_L \quad f_H = \frac{1}{2\pi C_{in} R'_{sig}}$	<p>Κοινού εκπομπού:</p> $f_H = \frac{\omega_0}{2\pi} = \frac{1}{2\pi C_{in} R'_{sig}}$ $R'_{sig} = r_\pi \parallel [r_x + (R_B \parallel R_{sig})] \quad R'_L = r_o \parallel R_C \parallel R_L$ $C_{in} = C_\pi + C_\mu(1 + g_m R'_L)$
--	--

$$\tau_H = C_{gs}R_{sig} + C_{gd}[R_{sig}(1 + g_m R'_L) + R'_L] + C_L R'_L$$

$$f_H \cong \frac{1}{2\pi\tau_H} \quad \omega_Z = g_m / C_{gd}$$

$$\omega_{P1} \cong \frac{1}{[C_{gs} + C_{gd}(1 + g_m R'_L)]R_{sig} + (C_L + C_{gd})R'_L}$$

$$\omega_{P2} = \frac{[C_{gs} + C_{gd}(1 + g_m R'_L)]R_{sig} + (C_L + C_{gs})R'_L}{[(C_L + C_{gd})C_{gs} + C_L C_{gd}]R'_L R_{sig}}$$

$$f_H \cong \frac{1}{2\pi C_{gd} R_{gd}} \quad |A_M| f_H = \frac{1}{2\pi C_{gd} R_{sig}}$$

Κοινής πύλης με ενεργό φορτίο:

$$f_{P1} = \frac{1}{2\pi C_{gs} \left(R_s \parallel \frac{1}{g_m + g_{mb}} \right)}$$

$$f_{P2} = \frac{1}{2\pi(C_{gd} + C_L)R_L}$$

$$f_H = \frac{1}{2\pi[C_{gs}R_{gs} + (C_{gd} + C_L)R_{gd}]}$$

Κοινής εκροής με ενεργό φορτίο:

$$\omega_Z = \frac{g_m}{C_{gs}}$$

$$f_H = \frac{1}{2\pi\tau_H} = 1/2\pi(C_{gd}R_{sig} + C_{gs}R_{gs} + C_L R_{CL})$$

Κοινού εκπομπού με ενεργό φορτίο:

$$A_M = -\frac{r_\pi}{R_{sig} + r_x + r_\pi}(g_m R'_L)$$

$$f_H \cong \frac{1}{2\pi C_{in} R'_{sig}}$$

$$\tau_H = C_\pi R'_{sig} + C_\mu[(1 + g_m R'_L)R'_{sig} + R'_L] + C_L R'_L$$

$$f_H \cong \frac{1}{2\pi\tau_H} \quad f_Z = \frac{1}{2\pi} \frac{g_m}{C_\mu}$$

$$f_{P1} \cong \frac{1}{2\pi} \frac{1}{[C_\pi + C_\mu(1 + g_m R'_L)]R'_{sig} + (C_L + C_\mu)R'_L}$$

$$f_{P2} \cong \frac{1}{2\pi} \frac{[C_\pi + C_\mu(1 + g_m R'_L)]R'_{sig} + (C_L + C_\mu)R'_L}{[C_\pi(C_L + C_\mu) + C_L C_\mu]R'_{sig} R'_L}$$

Κοινού συλλέκτη με ενεργό φορτίο:

$$\omega_Z = \frac{1}{C_\pi r_e}$$

$$f_H = 1/2\pi[C_\mu R_\mu + C_\pi R_\pi]$$

$$R_\mu = R'_{sig} \parallel [r_\pi + (\beta + 1)R'_L]$$

$$R_\pi = \frac{R'_{sig} + R'_L}{1 + \frac{R'_{sig}}{r_\pi} + \frac{R'_L}{r_e}}$$

$$R'_L = R_L \parallel r_o$$

$$R'_{sig} = R_{sig} + r_x$$

Πολυβάθμιοι ενισχυτές

$$A_v = e_{out}/V_s = A_1 A_2 \dots A_n \quad \frac{R_{in1}}{R_{in1} + R_s} \quad \frac{R_{in2}}{R_{in2} + R_{out1}} \quad \dots \quad \frac{R_L}{R_L + R_{outn}}$$

Με n όμοιες βαθμίδες: $\omega_{nL} = \frac{\omega_o}{\sqrt{2^{1/n} - 1}}$. Με n βαθμίδες με f_{Lj} , $j = 1, \dots, n$: $f_{nL} \approx 1.1 \sqrt{f_{L1}^2 + f_{L2}^2 + \dots + f_{Ln}^2}$

Με n όμοιες βαθμίδες: $\omega_{nH} = \omega_o \sqrt{2^{1/n} - 1}$. Με n βαθμίδες με f_{Hj} , $j = 1, \dots, n$: $f_{nH} \approx \frac{1}{1.1 \sqrt{\frac{1}{f_{H1}^2} + \frac{1}{f_{H2}^2} + \dots + \frac{1}{f_{Hn}^2}}}$

Ζεύγος κοινού συλλέκτη – κοινής βάσης:

$$\frac{V_o}{V_{sig}} = \frac{1}{2} \left(\frac{R_{in}}{R_{in} + R_{sig}} \right) (g_m R_L)$$

$$R_{in} = 2r_\pi$$

$$f_{P1} = \frac{1}{2\pi \left(\frac{C_\pi}{2} + C_\mu \right) (R_{sig} \parallel 2r_\pi)}$$

$$f_{P2} = \frac{1}{2\pi C_\mu R_L}$$

$$f_H \cong 1 / \sqrt{\frac{1}{f_{P1}^2} + \frac{1}{f_{P2}^2}}$$

Ζεύγος κοινής πηγής – κοινής πύλης (κασκοδική συνδεσμολογία):

$$R_{out} = r_{o2} + [1 + (g_{m2} + g_{mb2})r_{o2}]r_{o1}$$

$$A_v = -A_0^2 \frac{R_L}{R_L + A_0 r_o}$$

$$f_H \cong \frac{1}{2\pi\tau_H}$$

$$\tau_H = R_{sig} [C_{gs1} + C_{gd1}(1 + g_{m1}R_{d1})] + R_{d1}(C_{gd1} + C_{db1} + C_{gs2})$$

$$R_{gd1} = (1 + g_{m1}R_{d1})R_{sig} + R_{d1}$$

$$+ (R_L \parallel R_{out})(C_L + C_{gd2})$$

Ζεύγος Κοινού εκπομπού – κοινής βάσης (κασκοδική συνδεσμολογία):

$$A_M = -\frac{r_\pi}{r_\pi + r_x + R_{sig}} g_m (\beta r_o \parallel R_L)$$

$$R_{c1} = r_{o1} \parallel \left[r_{e2} \left(\frac{r_{o2} + R_L}{r_{o2} + R_L / (\beta_2 + 1)} \right) \right]$$

$$R'_{sig} = r_{\pi1} \parallel (r_{x1} + R_{sig})$$

$$R_{\pi1} = R'_{sig}$$

$$R_{\mu1} = R'_{sig}(1 + g_{m1}R_{c1}) + R_{c1}$$

$$f_H \cong \frac{1}{2\pi\tau_H}$$

$$\tau_H = C_{\pi1}R_{\pi1} + C_{\mu1}R_{\mu1} + (C_{cs1} + C_{\pi2})R_{c1} + (C_L + C_{cs2} + C_{\mu2})(R_L \parallel R_{out})$$

Τελεστικός ενισχυτής MOS δύο βαθμίδων:

$$A_v = -g_{m1}(r_{ds2} \parallel r_{ds4}) \quad g_{m1} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L} \right)_1 I_{D1}} = \sqrt{2\mu_p C_{ox} \left(\frac{W}{L} \right)_1 \frac{I_{bias}}{2}}$$

$$R_B = \frac{2}{\sqrt{2\mu_n C_{ox} (W/L)_{12} I_B}} \left(\sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} - 1 \right)$$

$$g_{m12} = \frac{2}{R_B} \left(\sqrt{\frac{(W/L)_{12}}{(W/L)_{13}}} - 1 \right)$$

$$g_{mi} = g_{m12} \sqrt{\frac{I_{Di} (W/L)_i}{I_B (W/L)_{12}}}$$

$$g_{mi} = g_{m12} \sqrt{\frac{\mu_p I_{Di} (W/L)_i}{\mu_n I_B (W/L)_{12}}}$$

$$C_1 = c_{gd4} + C_{db4} + C_{gd2} + C_{db2} + C_{gs6}$$

$$C_2 = C_{db6} + C_{db7} + C_{gd7} + C_L$$

$$\omega_Z = \frac{G_{m2}}{C_C}$$

$$\omega_{P1} = \frac{1}{C_1 R_1 + C_2 R_2 + C_C (G_{m2} R_2 R_1 + R_1 + R_2)} \cong \frac{1}{R_1 C_C G_{m2} R_2}$$

$$\omega_{P2} = \frac{G_{m2} C_C}{C_1 C_2 + C_C (C_1 + C_2)}$$

$$\omega_t = (G_{m1} R_1 G_{m2} R_2) \omega_{P1}$$

Επιλογή C_C ώστε $\omega_t < \omega_Z, \omega_{P2}$

$$PSRR = g_{mN}(r_{oP} \parallel r_{oN})$$

$$SR \equiv \frac{dV_{out}}{dt} \Big|_{\max} = \frac{I_{SS}}{C_L}$$

$$GB = A_v(0) \cdot |p_1| = (g_{m1} g_{m2} R_I R_{II}) \cdot \left(\frac{1}{g_{m2} R_I R_{II} C_c} \right) = \frac{g_{m1}}{C_c}$$

$$Arg[AB] = \pm 180^\circ - \tan^{-1} \left(\frac{\omega}{|p_1|} \right) - \tan^{-1} \left(\frac{\omega}{|p_2|} \right) - \tan^{-1} \left(\frac{\omega}{Z} \right)$$

Για περιθώριο φάσης 45° και $z \geq 10$ GB: $|p_2| \geq 1.22\text{GB}$

Για περιθώριο φάσης 60° και $z \geq 10$ GB: $|p_2| \geq 2.22\text{GB}$

$$Z = \frac{1}{C_c(1/g_{m2} - R_Z)}$$

Σχεδίαση Τελεστικού ενισχυτή MOS με είσοδο n-MOS

$$SR = \frac{I_5}{C_c} \quad A_{v1} = \frac{-g_{m1}}{g_{ds2} + g_{ds4}} = \frac{-2g_{m1}}{I_5(\lambda_2 + \lambda_4)} \quad A_{v2} = \frac{-g_{m6}}{g_{ds6} + g_{ds7}} = \frac{-g_{m6}}{I_6(\lambda_6 + \lambda_7)}$$

$$GB = \frac{g_{m1}}{C_c} \quad p_2 = \frac{-g_{m6}}{C_L} \quad Z = \frac{g_{m6}}{C_c} \quad \beta = K' \frac{W}{L} \cong \mu_0 C_{ox} \frac{W}{L} \quad (A/V^2)$$

$$V_{in(max)} = V_{DD} - \sqrt{\frac{I_5}{\beta_3}} - |V_{T03}|_{(max)} + V_{T01(min)} \quad V_{in(min)} = V_{ss} + \sqrt{\frac{I_5}{\beta_1}} + V_{T01(max)} + V_{DS5(sat)} \quad V_{DS(sat)} = \sqrt{\frac{2I_{DS}}{\beta}}$$

Για είσοδο

p-MOS: $V_{in(max)} = V_{DD} - \sqrt{\frac{I_5}{\beta_1}} - V_{DS5(sat)} - |V_{T01}|_{(max)} \quad V_{in(min)} = V_{ss} + \sqrt{\frac{I_5}{\beta_3}} + V_{T03(max)} - |V_{T01}|_{(min)}$

$$C_c > 0.22C_L \quad I_5 = SR \cdot C_c \quad S_3 = (W/L)_3 = \frac{I_5}{(K'_3)[V_{DD} - V_{in(max)} - |V_{T03}|_{(max)} + V_{T01(min)}]^2}$$

$$\frac{g_{m3}}{2C_{gs3}} > 10GB \quad g_{m1} = GB \cdot C_c \Rightarrow S_1 = S_2 = \frac{g_{m2}^2}{K'_2 I_5}$$

$$V_{DS5(sat)} = V_{in(min)} - V_{SS} - \sqrt{\frac{I_5}{\beta_1}} - V_{T01(max)} \geq 100mV \quad S_5 = \frac{2I_5}{K'_5[V_{DS5sat}]^2}$$

$$g_{m6} = 2.2g_{m2}(C_L/C_c) \quad S_6 = S_4 \frac{g_{m6}}{g_{m4}} \quad I_6 = \frac{g_{m6}^2}{2K'_6 S_6}$$

$$S_6 = \frac{g_{m6}}{K'_6 V_{DS6(sat)}} \quad V_{DS6} = V_{DS6(min)} = V_{DS6(sat)} = V_{DD} - V_{out(max)} \quad S_7 = (I_6/I_5)S_5$$

$$A_v = \frac{2g_{m2}g_{m6}}{I_5(\lambda_2 + \lambda_4)I_6(\lambda_6 + \lambda_7)} \quad P_{diss} = (I_5 + I_6)(V_{DD} + |V_{SS}|)$$

Κυκλώματα ανόρθωσης

$$V_Z = V_{Z0} + r_z I_Z$$

$P_{DC} = I_{DC}^2 R = \frac{I_m^2}{\pi^2} R$	$P_{AC} = I_{rms}^2 R = \frac{I_m^2}{4} R$	$n = \frac{P_{DC}}{P_{AC}} 100\% = 40.6\%$	$r = \frac{\sqrt{I_{rms}^2 - I_{DC}^2}}{I_{DC}} 100\% = 121\%$
$P_{DC} = I_{DC}^2 R = \frac{4I_m^2}{\pi^2} R$	$P_{AC} = I_{rms}^2 R = \frac{I_m^2}{2} R$	$n = \frac{P_{DC}}{P_{AC}} 100\% = 81.2\%$	$r = \frac{\sqrt{I_{rms}^2 - I_{DC}^2}}{I_{DC}} 100\% = 48\%$

Ημιανορθωτής με φίλτρο πυκνωτή:

$$V_{DC} \equiv V_O = V_p - \frac{1}{2} V_r \quad i_{D_{av}} = I_L (1 + \pi \sqrt{2V_p/V_r}) \quad i_{D_{max}} = I_L (1 + 2\pi \sqrt{2V_p/V_r})$$

$$V_r = \frac{V_p}{fCR} = \frac{I_L}{fC} \quad r = \frac{V_{AC(rms)}}{V_{DC}} = \frac{V_r}{2\sqrt{3}V_{DC}} \approx \frac{1}{2\sqrt{3}fCR}$$

Πλήρης ανορθωτής με φίλτρο πυκνωτή:

$$V_r = \frac{V_p}{2fCR} \quad i_{D_{av}} = I_L (1 + \pi \sqrt{V_p/2V_r}) \quad i_{D_{max}} = I_L (1 + 2\pi \sqrt{V_p/2V_r})$$

$$r = \frac{V_{AC(rms)}}{V_{DC}} = \frac{V_r}{2\sqrt{3}V_{DC}} \approx \frac{1}{4\sqrt{3}fCR}$$

Κυκλώματα αναφοράς

Πηγή Widlar:	$V_T \ln \frac{I_{IN}}{I_{OUT}} = I_{OUT} R_2$	$I_{OUT} R_2 + \sqrt{\frac{2I_{OUT}}{k'(W/L)_2}} - V_{ov1} = 0$ $\sqrt{I_{OUT}} = \frac{-\sqrt{\frac{2}{k'(W/L)_2}} + \sqrt{\frac{2}{k'(W/L)_2} + 4R_2 V_{ov1}}}{2R_2}$
Πηγή μεγίστου ρεύματος:	$I_{OUT} = I_{IN} \exp\left(-\frac{I_{IN} R}{V_T}\right)$ $R = \frac{V_T}{I_{IN}} \ln \frac{I_{IN}}{I_{OUT}}$	$I_D = \frac{W}{L} I_t \exp\left(\frac{V_{GS} - V_t}{nV_T}\right) \left[1 - \exp\left(-\frac{V_{DS}}{V_T}\right)\right]$ $I_{OUT} \approx \frac{W}{L} I_t \exp\left(\frac{V_{GS2} - V_t}{nV_T}\right) \approx I_{IN} \exp\left(-\frac{I_{IN} R}{nV_T}\right)$ $I_{OUT} = \frac{k'(W/L)_2}{2} (V_{ov2})^2 = \frac{k'(W/L)_2}{2} (V_{ov1} - I_{IN} R)^2$

$$S_{V_{SUP}}^{I_{OUT}} = \frac{V_{SUP}}{I_{OUT}} \frac{\partial I_{OUT}}{\partial V_{SUP}}$$

$$S_{V_{CC}}^{I_{OUT}} = \left(\frac{1}{1 + \frac{I_{OUT} R_2}{V_T}} \right) \frac{V_{CC}}{I_{IN}} \frac{\partial I_{IN}}{\partial V_{CC}} = \left(\frac{1}{1 + \frac{I_{OUT} R_2}{V_T}} \right) S_{V_{CC}}^{I_{IN}}$$

$$S_{V_{DD}}^{I_{OUT}} = \frac{V_{ov1}}{\sqrt{V_{ov2}^2 + 4I_{OUT}R_2V_{ov1}}} S_{V_{DD}}^{I_{IN}}$$

$$TC_F = \frac{1}{I_{OUT}} \frac{\partial I_{OUT}}{\partial T} = \frac{1}{V_{BE1}} \frac{\partial V_{BE1}}{\partial T} - \frac{1}{R} \frac{\partial R}{\partial T}$$

$$TC_F = \frac{1}{I_{OUT}} \frac{\partial I_{OUT}}{\partial T} \simeq \frac{1}{V_t} \frac{\partial V_t}{\partial T} - \frac{1}{R} \frac{\partial R}{\partial T}$$

$$TC_F = \frac{1}{I_{OUT}} \frac{\partial I_{OUT}}{\partial T} = \frac{1}{V_T} \frac{\partial V_T}{\partial T} - \frac{1}{R_2} \frac{\partial R_2}{\partial T}$$

$$V_{OUT} = V_{BE(on)} + MV_T$$

$$V_{OUT} = V_{G0} + V_T(\gamma - \alpha) \left(1 + \ln \frac{T_0}{T} \right)$$

$$V_{OUT} = V_{BE2} + V_{R3} + V_{R2} = V_{BE2} + \left(1 + \frac{R_2}{R_3} \right) \Delta V_{BE}$$

$$= V_{BE2} + \left(1 + \frac{R_2}{R_3} \right) V_T \ln \frac{R_2 I_{S2}}{R_1 I_{S1}} = V_{BE2} + MV_T$$

Ενισχυτές Ισχύος

Τάξη Α:

$$P_L = \frac{(\hat{V}_o/\sqrt{2})^2}{R_L} = \frac{1}{2} \frac{\hat{V}_o^2}{R_L}$$

$$P_S = 2V_{CC}I$$

$$\eta = \frac{1}{4} \frac{\hat{V}_o^2}{IR_L V_{CC}} = \frac{1}{4} \left(\frac{\hat{V}_o}{IR_L} \right) \left(\frac{\hat{V}_o}{V_{CC}} \right)$$

Τάξη Β:

$$P_L = \frac{1}{2} \frac{\hat{V}_o^2}{R_L} \quad P_{S+} = P_{S-} = \frac{1}{\pi} \frac{\hat{V}_o}{R_L} V_{CC} \quad P_S = \frac{2}{\pi} \frac{\hat{V}_o}{R_L} V_{CC}$$

$$\eta = \left(\frac{1}{2} \frac{\hat{V}_o^2}{R_L} \right) / \left(\frac{2}{\pi} \frac{\hat{V}_o}{R_L} V_{CC} \right) = \frac{\pi}{4} \frac{\hat{V}_o}{V_{CC}}$$

$$\eta_{\max} = \frac{\pi}{4} = 78.5\%$$

$$P_{L\max} = \frac{1}{2} \frac{V_{CC}^2}{R_L}$$

$$P_{DN\max} = P_{DP\max} = \frac{V_{CC}^2}{\pi^2 R_L}$$

Τάξη AB:

$$v_O = v_I + \frac{V_{BB}}{2} - v_{BEN}$$

$$i_N^2 - i_L i_N - I_Q^2 = 0$$

$$R_{out} = \frac{V_T}{i_N} \parallel \frac{V_T}{i_P} = \frac{V_T}{i_P + i_N}$$

$$T_J \simeq T_A = \theta_{JA} P_D$$

$$\theta_{JA} = \frac{T_{J\max} - T_{A0}}{P_{D0}}$$

$$P_{D\max} = \frac{T_{J\max} - T_C}{\theta_{JC}}$$

$$\theta_{JA} = \theta_{JC} + \theta_{CA}$$

$$\theta_{CA} = \theta_{CS} + \theta_{SA}$$

$$T_J - T_A = P_D (\theta_{JC} + \theta_{CS} + \theta_{SA})$$

Ηλεκτρονικά ελέγχου ισχύος

$$V_{da}^h = \frac{1}{2\pi} \int_a^\pi V_{sm} \sin(\omega_s t) d(\omega_s t) = \frac{V_{sm}}{\pi} \left[\frac{1 + \cos a}{2} \right] = V_{do}^h \left[\frac{1 + \cos a}{2} \right]$$

$$I_d = \frac{1}{2\pi R} \int_a^{\pi-\delta} (V_{sm} \sin \omega_s t - V_B) d(\omega_s t) \quad \delta = \sin^{-1}(V_B / V_{sm}) \quad \delta < a < \pi - \delta$$

$$V_{da}^f = \frac{1}{\pi} \int_a^\pi V_{sm} \sin(\omega_s t) d(\omega_s t) = \frac{V_{sm}}{\pi} (1 + \cos a)$$

$$V_{da}^f = \frac{1}{\pi} \int_a^{\pi+a} V_{sm} \sin(\omega_s t) d(\omega_s t) = \frac{2V_{sm}}{\pi} \cos a = V_{do}^f \cos a \quad \cos \phi_1 = \cos a$$

$$PF = \frac{I_{s1}}{I_s} \cos \phi_1 = \frac{2\sqrt{2}}{\pi} \cos a \quad P_s = V_s I_{s1} \cos \phi_1 = V_{da}^f I_d = \frac{2V_{sm}}{\pi} I_d \cos a$$

$$V_{da}^f = \frac{1}{\pi} \int_a^{\pi+a} V_{sm} \sin(\omega_s t) d(\omega_s t) = \frac{2V_{sm}}{\pi} \cos a = V_{do}^f \cos a \quad 0 < a < \cos^{-1} \left\{ \frac{V_B \pi}{2V_{sm}} \right\} \quad I_d = \frac{V_{da}^f - V_B}{R}$$

$$P_B = V_B I_d$$

$$P_{d|a>\pi/2} = P_s = V_{da}^f I_d = V_{do}^f I_d \cos a = V_s I_{s1} \cos \phi_1 < 0 \quad I_d = \frac{V_{da}^f - V_B}{R} \quad V_{da}^f = V_{do}^f \cos a$$